

Boolean algebra and logic circuits — logic you can build

Lesson 4 · Module 0 — Logic, Circuits & Proof · Discrete Mathematics · dailymaths.uk/discrete

Practice problems

1. A circuit has two inputs p and q . The inputs are fed into a NAND gate, and the output of that gate is then fed into a NOT gate. Write the final boolean expression and simplify it.
2. Construct the boolean expression for a circuit that outputs 1 if and only if exactly one of the two inputs p and q is 1 (the XOR function) using only AND, OR, and NOT gates.
3. A security system triggers an alarm ($A = 1$) if the master switch ($S = 1$) is on AND (either the door sensor ($D = 1$) is triggered OR the window sensor ($W = 1$) is triggered). Write the boolean expression and determine the output if $S = 1, D = 0, W = 1$.

Solutions

1. A circuit has two inputs p and q . The inputs are fed into a NAND gate, and the output of that gate is then fed into a NOT gate. Write the final boolean expression and simplify it.

- The NAND gate output is $\overline{p \cdot q}$.
- The NOT gate negates this output: $\overline{\overline{p \cdot q}}$.
- Using the double negation law, $\overline{\overline{A}} = A$.
- The expression simplifies to $p \cdot q$.

Answer: $p \cdot q$

2. Construct the boolean expression for a circuit that outputs 1 if and only if exactly one of the two inputs p and q is 1 (the XOR function) using only AND, OR, and NOT gates.

- Exactly one is 1 means: (p is 1 AND q is 0) OR (p is 0 AND q is 1).
- Translate this to boolean algebra: $(p \cdot \bar{q}) + (\bar{p} \cdot q)$.
- This uses two NOT gates, two AND gates, and one OR gate.

Answer: $(p \cdot \bar{q}) + (\bar{p} \cdot q)$

3. A security system triggers an alarm ($A = 1$) if the master switch ($S = 1$) is on AND (either the door sensor ($D = 1$) is triggered OR the window sensor ($W = 1$) is triggered). Write the boolean expression and determine the output if $S = 1, D = 0, W = 1$.

- The condition 'either door or window' is $D + W$.
- The master switch condition is $S \cdot (D + W)$.
- Substitute the values: $1 \cdot (0 + 1)$.
- Evaluate the parentheses: $1 \cdot 1 = 1$.

Answer: $A = S \cdot (D + W)$; Output is 1